

Name _____

AST 363 - Exam 1

Part 1 Closed Book

Multiple Choice: 2 pt. each

1. The maximum instantaneous voltage to ground occurring on a 120/240 v single phase system is about:
 - a) 240 V
 - b) 120 V
 - c) this depends on the type of meter used.
 - d) 170 V
 - e) 0 V
 - f) 84.6 V
 - g) 115 V

2. In an AC circuit, power is used by
 - a) resistances
 - b) capacitances
 - c) inductances
 - d) all of the above
 - e) (a) & (b)
 - f) (a) & (c)
 - g) (b) & (c)

3. When an extra series load is added to a series circuit,
 - a) voltages across and currents through other loads are not changed.
 - b) voltages change, but currents remain the same.
 - c) currents change, but voltages remain the same.
 - d) voltages across and currents through other loads change.

4. Cone heater resistances measured with the resistance meter were less than resistances computed using current and voltage readings because
 - a) meters tend to read low on the resistance scale.
 - b) DC resistance is less than AC resistance.
 - c) of resistance of the conductors leading to the cone heater
 - d) resistance of metal goes up as temperature increases.

5. An ammeter placed in parallel with a load will
- a) read correctly the current through the load.
 - b) shut off almost all the current to the load.
 - c) cause a short circuit, but no damage to the meter.
 - d) cause a short circuit and possibly ruin the meter.
 - e) read correctly the voltage across the load
 - f) rrectly the voltage across the load.
6. The RMS value is shown on the dial of most AC meters because
- a) this is the only practical way to construct a meter.
 - b) use of the RMS value permits calculation of power in AC and DC circuits using the same formula.
 - c) this is a strong tradition among meter manufacturers.
 - d) a meter which reads in RMS values will last much longer than one reading peak or squared values.
7. The power factor,
- a) is a measure of how much energy the electrons contain while moving along a conductor.
 - b) has units called vombs and is the power in watts multiplied by the resistance in ohms.
 - c) is less than 1.0 if more current is flowing to the load than is required supply the actual power used by the load.
 - d) is a measure of efficiency and is the output power divided by the input power.
8. The volt amps drawn by a load equal the watts drawn by the load -
- a) always
 - b) never
 - c) when $PF < 1$
 - d) when $PF > 1$
 - e) when PF
 - f) 1
9. A certain load operates with a power factor of 0.8. A resistance is placed in parallel with this load. The power factor of the combined load is:
- a) 0.8
 - b) < 0.8
 - c) > 0.8
 - d) b or c depending on whether original power factor was leading or lagging.


10. How long will it take a 4kW load to use 12 kWh of energy?
- a) 3 hour
 - b) 1/3 hour
 - c) 36 minutes
 - d) 3.6 hours
 - e) none of the above
11. When a circuit breaker-type ground fault interrupter trips, the circuit neutral is opened,
- a) true
 - b) false
 - c) depends on brand of device.
12. A GFI will NOT protect a person who contacts
- a) red conductor and earth
 - b) black conductor and earth
 - c) black conductor and neutral conductor
13. An electric shock victim has gone into ventricular fibrillation.
- a) there is no way to prevent death.
 - b) the person might be revived by professional treatment if kept alive until arrives.
 - c) the person will come out of fibrillation spontaneously if kept alive by CPR.
 - d) this occurs from most shocks and is not considered a dangerous situation.
14. The rotor in a watthour meter
- a) turns at a constant speed whenever a load is on.
 - b) turns at a constant speed all the time.
 - c) turns at a speed proportional to the load.
 - d) varies in speed in a manner not related to the load.
15. In a service entrance panel, the neutral is normally
- a) not switched or overcurrent protected
 - b) overcurrent protected, but not switched
 - c) switched but not overcurrent protected
 - d) switched and overcurrent protected
 - e) not brought in because box is grounded
16. In order to switch a light from 4 locations, these switches are needed:
- a) 2-S, 2-S3
 - b) 2-S3, 2-S4
 - c) 4-S4
 - d) 1-S4, 3-S3

- (10) 17. Draw the circuit of a service transformer which reduces distribution line voltages down to voltages usable for common electrical loads. Indicate all connections to earth, and all wire colors that are commonly used.

Part 2 Open book & notes

Name _____

18. (9)

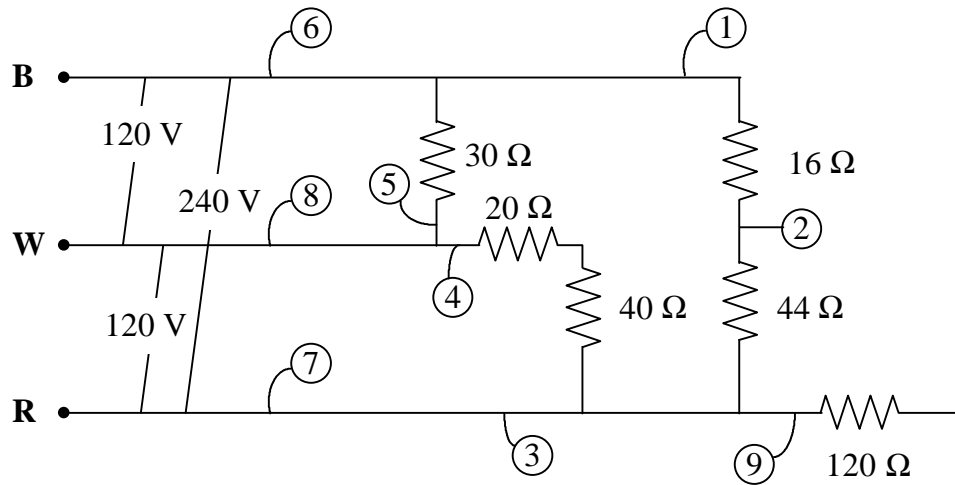

Compute:

I_1

I_2

I_3

I_4

I_5


I_6

I_7

I_8

I_9

20. (15)

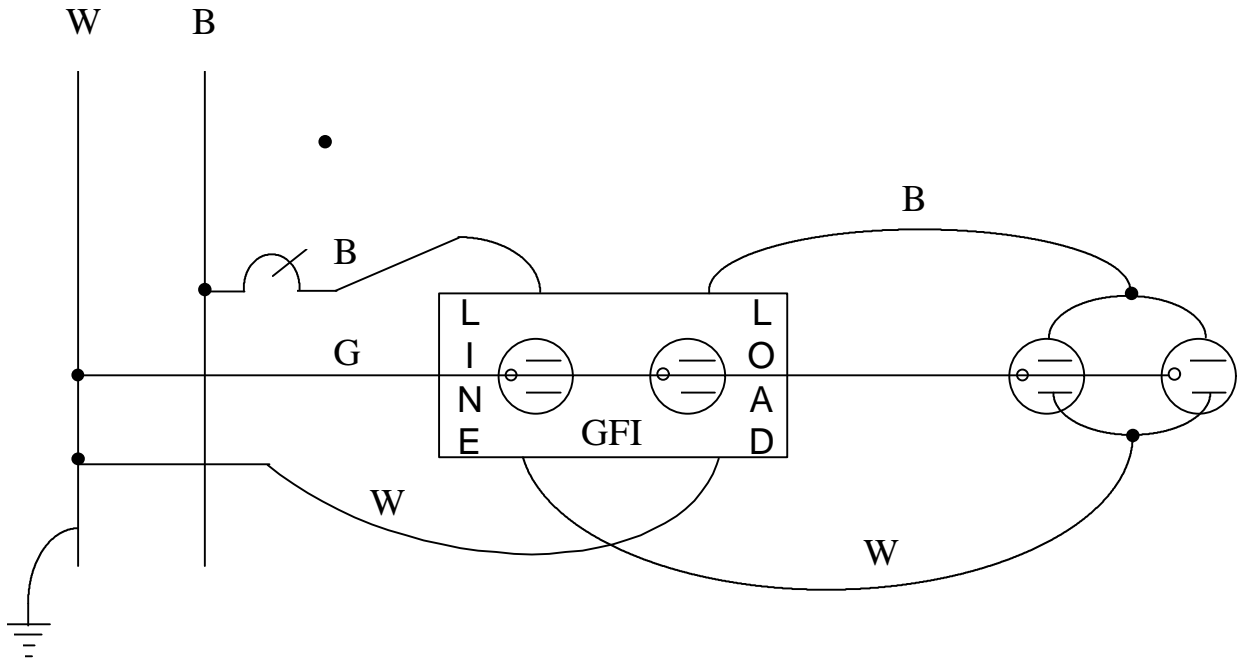

A GFI is wired as shown. Using your knowledge of GFI operation, explain what will happen in each case, and why:


Case 1 A load, but no ground fault on the GFI receptacle.

Case 2 A load but no ground fault on the conventional receptacle.

Case 3 A ground fault but no load on the GFI receptacle.

Case 4 A ground fault but no load on the conventional receptacle.

21. (10)

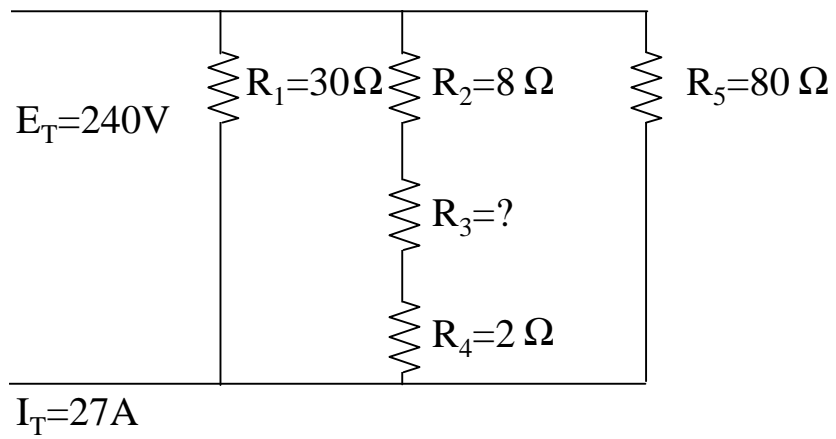

Compute the value of R_3 .

What power is used by R_4 ?

What is the equivalent resistance of the entire circuit?